

Reversible Quantum Ripple Carry Adders

Advanced Architectures



SAPIENZA
UNIVERSITÀ DI ROMA

Andrea Di Marco (1835169)
Jemuel Espiritu Fuentes (1803530)




SAPIENZA
UNIVERSITÀ DI ROMA

Introduction



Introduction

- We implemented four **quantum ripple-carry adders**.
 - And some variations.
- In this presentation we consider **5-bit** adders.
 - We made a **generalized generator** on Python.
- We used both **Qiskit** and **QASM** for the implementation.
- We are first going to explain the adders individually.
- At the end we will show a **comparison of all the adders**.
 - Using **standard metrics** that allow to highlight the strengths and weaknesses of each adder.

 




Efficient Addition


- Reversible adders are essential circuits in quantum computing systems.
- **Shor's factoring algorithm** is one of the most prominent examples in which reversible arithmetic is needed.
 - The most intensive part of the algorithm is **exponentiation**.
 - The usual approach uses **multiplier** circuits, constructed using adders.
- For this reason there is a great interest in the creation of new designs and the perfection of the existing ones.
- Some methodologies focus on minimizing the **necessary resources**, others on optimizing **computing time**, etc.
 - Compromises are required.

Ripple-Carry Addition

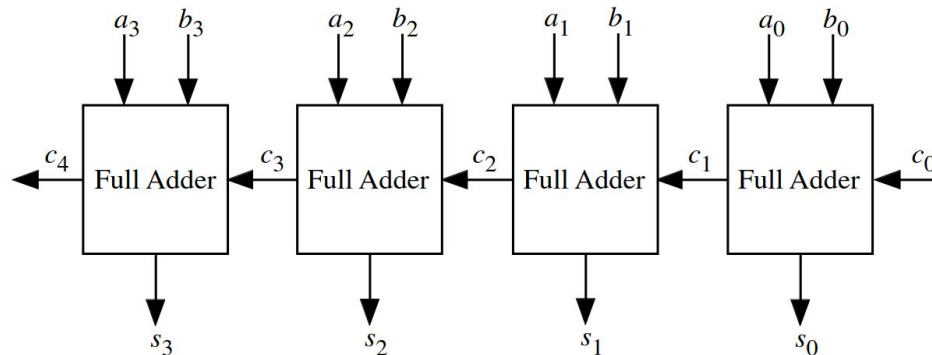- A one-bit **full adder** is a combinational circuit that forms the arithmetic sum of three bits.
 - It consists of three inputs and two outputs
- A n -bit ripple-carry adder is built chaining n full adders, connecting the c_{out} output of every full adder with the c_{in} input of the next full adder.



 - Carry-lookahead adders precompute the carry in advance but the **carry logic block** gets very complicated for more than 4 bits



Qiskit

- Qiskit is an open-source **software development kit (SDK)** for working with quantum computers at the level of circuits, pulses, and algorithms.
- Provides tools for creating and manipulating quantum programs and running them on **real quantum devices** on IBM Quantum Platform or on **simulators** on a local computer.

```
circuit.h(qreg_q[2])
circuit.t(qreg_q[2])
circuit.barrier(qreg_q[0], qreg_q[1], qreg_q[2])
circuit.cx(qreg_q[0], qreg_q[2])
circuit.cx(qreg_q[1], qreg_q[2])
circuit.cx(qreg_q[2], qreg_q[0])
circuit.cx(qreg_q[2], qreg_q[1])
circuit.barrier(qreg_q[0], qreg_q[1], qreg_q[2])
circuit.t(qreg_q[2])
circuit.tdg(qreg_q[0])
circuit.tdg(qreg_q[1])
circuit.cx(qreg_q[2], qreg_q[0])
circuit.cx(qreg_q[2], qreg_q[1])
circuit.h(qreg_q[2])
circuit.s(qreg_q[2])
```



QASM

- Open Quantum Assembly Language (*OpenQASM*) is a **programming language** designed for describing quantum circuits and algorithms for execution on quantum computers.
- Allows to define custom gates.
- Can also be **simulated** with the Qiskit libraries.

```
gate lAND a, b, c {  
  cx a, c;  
  cx b, c;  
  cx c, a;  
  cx c, b;  
  barrier a;  
  t c;  
  tdg a;  
  tdg b;  
  cx c, b;  
  cx c, a;  
  h c;  
  s c;  
}  
  
qreg q[14];  
creg c[1];
```



IBM Quantum Learning

Catalog

Composer




Edit

View

Visualizations seed

7166




Setup and run 





Left alignment



Inspect ☐

 

Statevector

 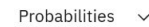

Privacy

Cookie preferences

Support






SAPIENZA
UNIVERSITÀ DI ROMA

Nagamani

2014

 

(b) quantum implementation of Toffoli gate


Introduction

- This work proposes a reversible quantum ripple-carry adder, optimized for **quantum cost** and **delay** and with **zero garbage outputs**.
- An operation is said to be **physically reversible** if it converts no energy to heat and produces no entropy.
- A reversible gate has the same number of input and output lines *i.e.*, for each output pattern there must be a **unique** input pattern.
- The Quantum Cost of a **Positive controlled Toffoli gate** is 5 and the delay associated with it is 5Δ .
- The Quantum Cost of a **Negative controlled Toffoli gate** is 6 with a delay of 6Δ .



1-bit Reversible Full Adder

 - The base module for this ripple-carry adder is the following *1-bit adder*:



- This block computes the sum and the carry out as

$$\text{Sum} = C \oplus B \oplus A$$

$$\text{Cout} = 0 \oplus (B \wedge C) \oplus (A \wedge (C \oplus B))$$

- The proposed design is simple and has
 - 4 gate count
 - 0 garbage outputs.




***n*-bit Reversible Full Adder**

- The methodology adapted is to ripple the carry through each stage of full adder circuits.
- The proposed 1-bit full adder circuit has been cascaded to work as a 4-bit reversible full adder.
- For each stage of input, 1 **ancilla input** is required producing no garbage output.
- The quantum cost of the proposed design is **$12n$** with a delay of **$10n\Delta$** .




4-bit Reversible Full Adder (2)

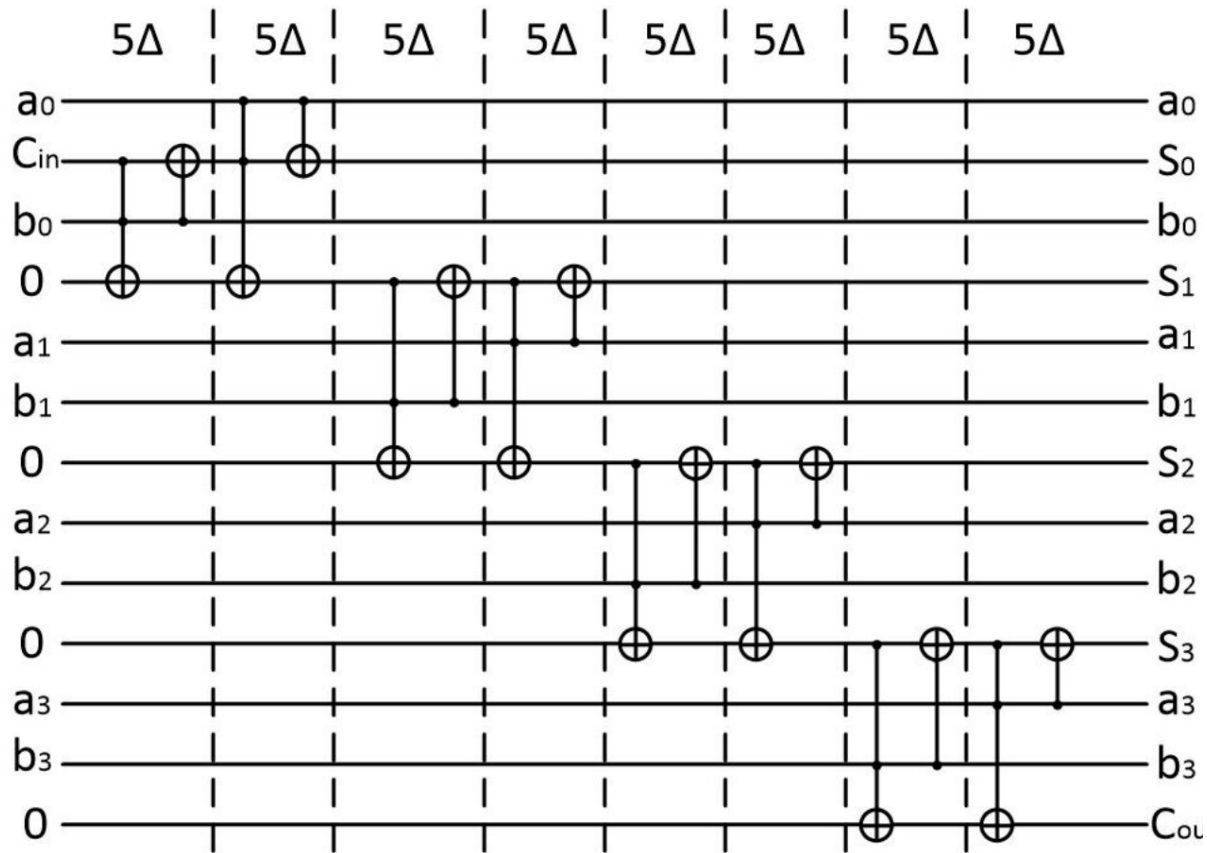



5-bit Reversible Full Adder (3)


 
- QC: $12n = 60$
- Delay: $10n\Delta = 50\Delta$





Negative Control Line Toffoli



- From Schönborn et al. (2014)

  



Negative Control Line Toffoli (2)


- From Schönborn et al. (2014)

  



n-bit Reversible Full (unsigned) Subtractor

 - Designed using the concept of **negative control lines**. This allows replacing series of gates and thereby reducing the area, gate count and as well as power consumption.
- All parameters such as ancilla **inputs** and **garbage outputs** remain the same as the full adder.



- The borrow-out formula is:
$$\text{Bout} = 0 \oplus (C \wedge B) \oplus (\neg A \wedge (C \oplus B))$$



Practical Example

- The borrow-out formula is:

$$o_i = 0 \oplus (b_i \wedge o_{i-1}) \oplus (\neg a_i \wedge (b_i \oplus o_{i-1}))$$

- Example:*

$$\begin{array}{l} A = 1 \ 0 \ 1 \\ B = 0 \ 1 \ 0 \end{array}$$

$$a_0 - b_0 = a_0 \oplus b_0 = 1$$

$$o_0 = 0$$

$$a_1 - b_1 = a_1 \oplus b_1 \oplus o_0 = 1$$


$$o_1 = 1$$

$$a_2 - b_2 = a_2 \oplus b_2 \oplus o_1 = 0$$

$$o_2 = 0$$




4-bit Subtractor

 



5-bit Subtractor (2)

 - QC: $13n = 65$
- Delay: $11n\Delta = 55\Delta$





SAPIENZA
UNIVERSITÀ DI ROMA

Gidney

2018



Introduction

- This adder makes use of *temporary logical-AND* blocks.
- The goal is to minimize the overall **T-count** for the addition, since this reduces the T-count of any construction based on addition.
- This adder requires a high number of **ancilla bits** which might hinder its implementation in small systems.
- This adder is **fault tolerant**.




Surface Codes

- Surface codes are a likely necessity in future quantum computers.
- They involve the arrangement of qubits into **two-dimensional lattices**.
- There are different surface code families with distinct properties and applications.
- Surface Codes allow for **quantum error correction**.
- **T gates** dominate the cost of quantum computation based on the surface code
- For this reason **temporary logical-ANDs** can represent a significant reduction in projected costs of quantum computation.





Surface Codes (2)

 - A simple example is grouping the qubits in **plaquettes**.
- And perform a **parity check** for each plaquette to detect errors:



  - The subsequent **error correction** phase requires many Toffoli gates.
 - Beyond the scope of this presentation.




Phase Errors

- The textbook construction of a Toffoli gate uses **seven T gates**.
- When a Toffoli operation is later un-computed by a second Toffoli operation, each gate in the pair can omit **three of the T gates** from the textbook construction.
- This introduces **phase errors** but the second Toffoli gate can uncompute the errors.
- Assuming **intermediate operations** aren't sensitive to the phase errors
- It is proven that a Toffoli gate requires **at least 4 T gates**, but it might be possible that n Toffolis could be implemented with fewer than $4n$ T gates for some n .



logical-AND construction

- The computation circuit has a **T-count** of 4.
- The $|T\rangle$ state input contributes to the T-count.

 


- *Practical example...*



logical-AND uncomputation

 - The uncomputation requires **only Clifford gates**.
- Has a T-count of **zero**.
- **Faster** than the logical-AND computation.
- Can also be done with the same gates as before.





$|T\rangle$

- Distilling this state can be an issue as it is a potential bottleneck since there is no cheap mechanism to apply **non-Clifford** operations such as T gates.
- $|T\rangle = \frac{1}{\sqrt{2}}(|0\rangle + e^{i\pi/4}|1\rangle)$
- On *Qiskit* it can be generated with:





5-bit Adder Construction

i_0 -

t_0 -

i_1 -

t_1 -

i_2 -

t_2 -

i_3 -

t_3 -

i_4 -

t_4 -

- i_0

- $(t + i)_0$

- i_1

- $(t + i)_1$

- i_2

- $(t + i)_2$

- i_3


- $(t + i)_3$

- i_4

- $(t + i)_4$



5-bit Adder Construction (2)

 

- i_0
- $(t + i)_0$

- i_1
- $(t + i)_1$


- i_2
- $(t + i)_2$

- i_3
- $(t + i)_3$

- i_4
- $(t + i)_4$




5-bit Adder Construction (3)

 



5-bit Addition


- *T count:*
- *QC:*
- *Delay:*

 



5-bit Addition

 
- ***T count:*** $4(n-1) = 16$
- ***QC:***
- ***Delay:***





5-bit Addition

 
- ***T count:*** $4(n-1) = 16$
- ***QC:*** 13
- ***Delay:***





5-bit Addition

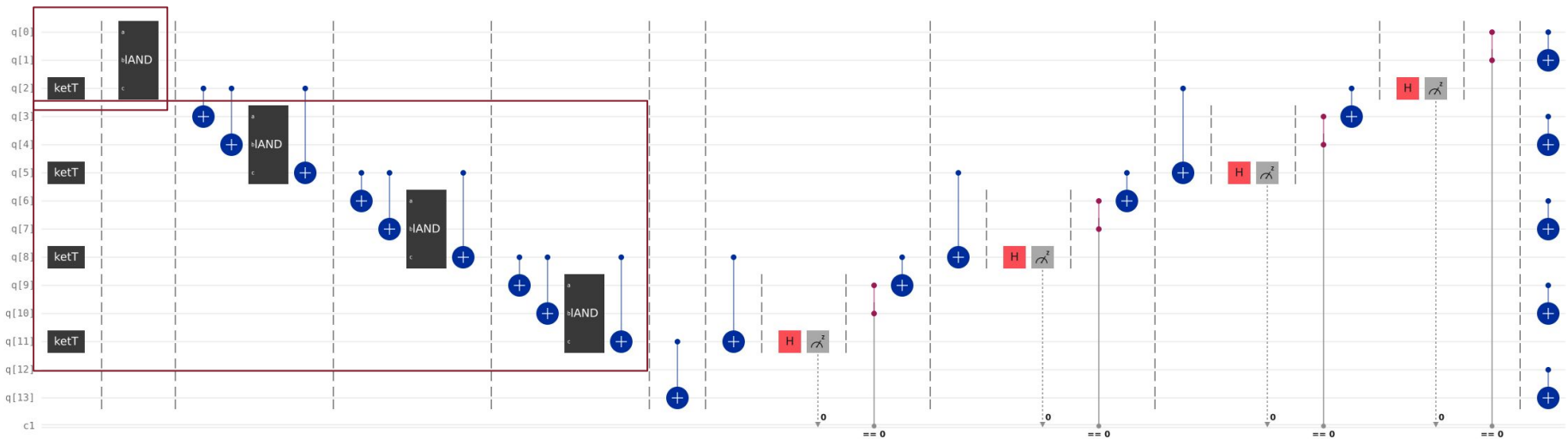
- ***T count:*** $4(n-1) = 16$
- ***QC:*** $13 + 48$
- ***Delay:***





5-bit Addition

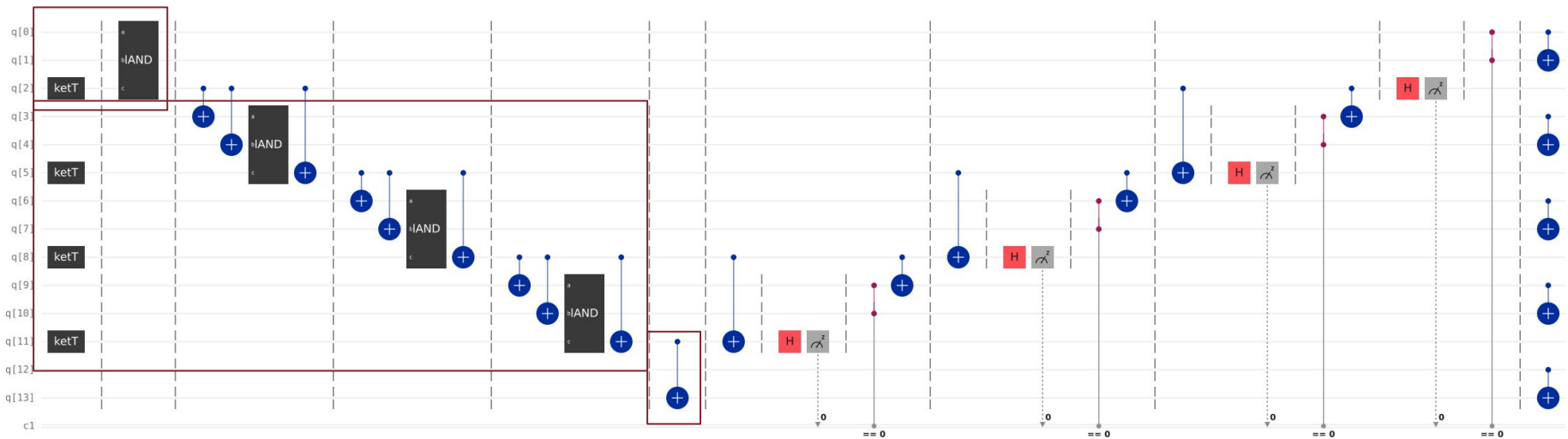
- ***T count***: $4(n-1) = 16$
- ***QC***: $13 + 48 + 1$
- ***Delay***:





5-bit Addition

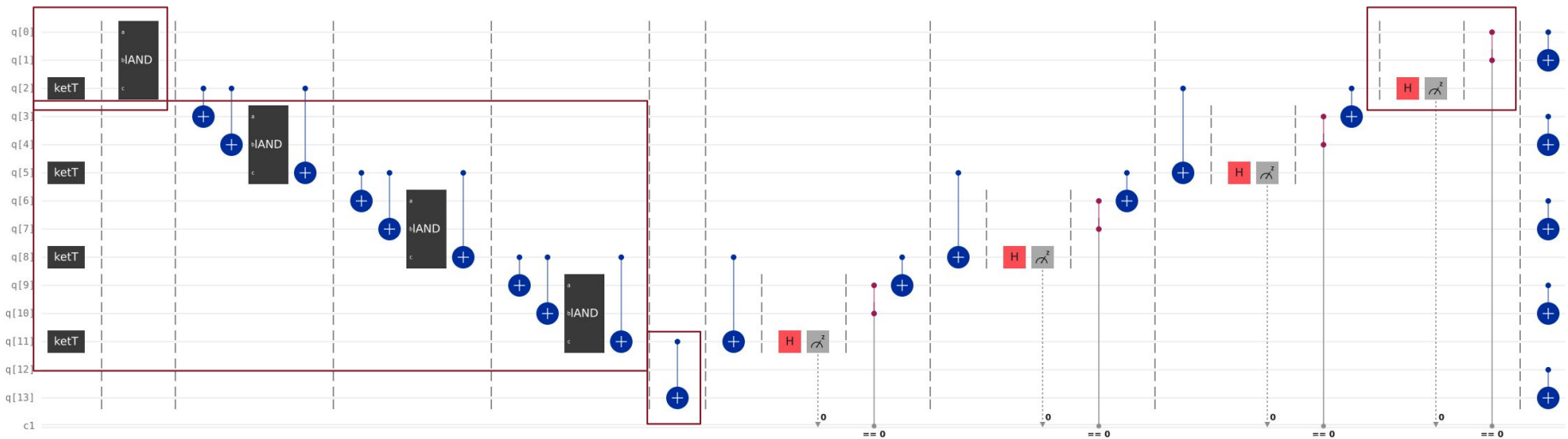
- ***T count:*** $4(n-1) = 16$
- ***QC:*** $13 + 48 + 1 + 3$
- ***Delay:***





5-bit Addition

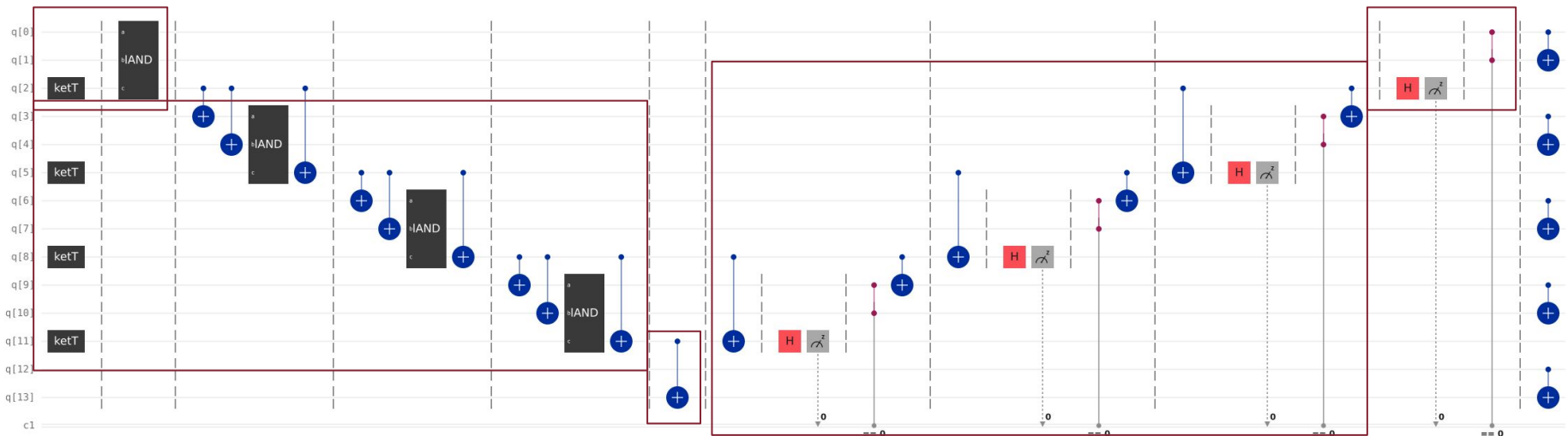
- ***T count***: $4(n-1) = 16$
- ***QC***: $13 + 48 + 1 + 3 + 15$
- ***Delay***:





5-bit Addition

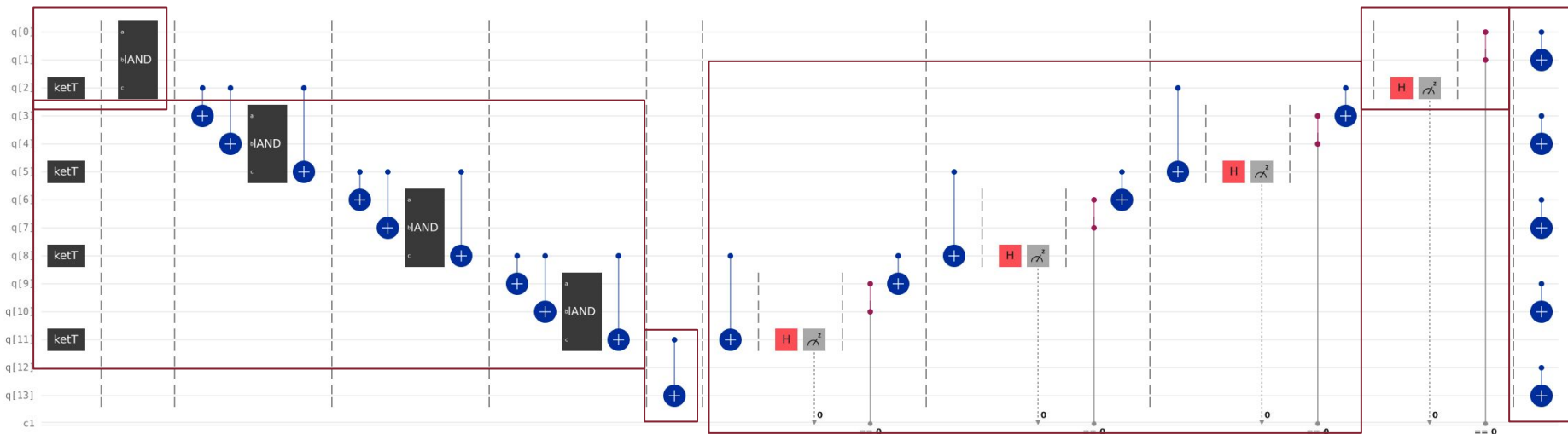
- ***T count***: $4(n-1) = 16$
- ***QC***: $13 + 48 + 1 + 3 + 15 + 5 = 85$
- ***Delay***:





5-bit Addition

 
- ***T count:*** $4(n-1) = 16$
- ***QC:*** 85
- ***Delay:*** 2





5-bit Addition

 
- ***T count***: $4(n-1) = 16$
- ***QC***: 85
- ***Delay***: $2 + 7$





5-bit Addition

 
- ***T count:*** $4(n-1) = 16$
- ***QC:*** 85
- ***Delay:*** $2 + 7 + 3$





5-bit Addition

 
- ***T count:*** $4(n-1) = 16$
- ***QC:*** 85
- ***Delay:*** $2 + 7 + 3 + 46$





5-bit Addition

 - ***T count***: $4(n-1) = 16$
- ***QC***: 85
- ***Delay***: $2 + 7 + 3 + 46 + 1 = 59$





SAPIENZA
UNIVERSITÀ DI ROMA


Takahashi

2010



Introduction

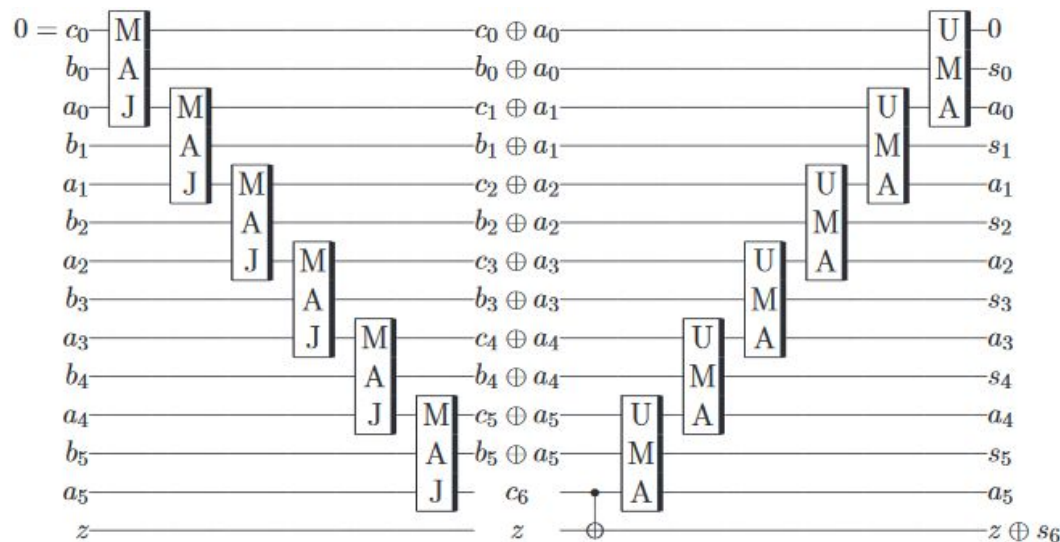- The work implements a quantum circuit for the **addition** of two binary numbers.
- The circuit follows a **ripple carry approach** and has $O(n)$ **depth** and $O(n)$ **size**
- It requires $2N+1$ **qubits** with N being the number of bits of the addends
 - No **ancilla** or **garbage** bits!
- It is partially based on the following adder by Cuccaro et al. (2004)





The Main Idea

- The problem of constructing quantum adder can be expressed as

$$\left(\bigotimes_{i=0}^{n-1} |b_i\rangle |a_i\rangle \right) |z\rangle \rightarrow \left(\bigotimes_{i=0}^{n-1} |s_i\rangle |a_i\rangle \right) |z \oplus s_n\rangle$$

- The Ripple Carry Approach requires the computation of the carry bits c_i

$$c_i = \begin{cases} 0 & i = 0, \\ \text{MAJ}(a_{i-1}, b_{i-1}, c_{i-1}) & 1 \leq i \leq n \end{cases} \quad (\text{MAJ}(a, b, c) = ab \oplus bc \oplus ca)$$


- And by having the carry we can compute s_i

$$s_i = \begin{cases} a_i \oplus b_i \oplus c_i & 0 \leq i \leq n-1, \\ c_n & i = n. \end{cases}$$



The Main Idea

 - Cuccaro uses an **ancillary** bit to store c_0 and uses the following gate in the circuit to produce the carry:



- In order to **avoid using the ancilla**, the Takahashi divides the MAJ gates in **2 parts**:
 - The 2 CNOT's
 - The Toffoli gate



The Main Idea


- using **CNOT gates** (the first parts of the MAJ gate) and a **Toffoli gate**, we first prepare the following state

$$|b_1 \oplus a_1\rangle |a_1 \oplus c_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus a_i\rangle |a_i \oplus a_{i-1}\rangle \right) |z \oplus a_{n-1}\rangle.$$

- By applying CCNOT gates, we can **compute** c_i and **store** it in the qubit initially **storing** a_i . The final Toffoli gate computes the **carry out** c_n and stores it in the **qubit** for z .
- The CCNOT maps
 - $|b_i \oplus a_i\rangle |a_i \oplus c_i\rangle |a_{i+1} \oplus a_i\rangle$ to $|b_i \oplus a_i\rangle |a_i \oplus c_i\rangle |a_{i+1} \oplus c_{i+1}\rangle$
- Then we first compute the $b_i \oplus c_i$ (with c_i stored in the qubit of a_i)
- Finally we bring back a_i and **do the last sum** to obtain the various s_i




Takahashi - Circuit (N = 5)

 



Step By Step Creation

 - Step 1:
 - apply CNOT gates to each B_i and A_i for $i=n-1, \dots, 1$ with A_i as **control**




The system state is now represented by this model:

$$|b_0\rangle|a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus a_i\rangle|a_i\rangle \right) |z\rangle$$



Step By Step Creation

 - Step 2:
 - apply CNOT gates to each A_{i+1} and A_i for $n=1, \dots, n-1$ with A_i as control





Step By Step Creation

- Step 2:
 - apply CNOT gates to each A_{i+1} and A_i for $n=1, \dots, n-1$ with A_i as **control**
- The CNOT is in fact **not applied** to the first two qubits A_0 and A_1 and the state evolves to the following:


$$|b_0\rangle|a_0\rangle|b_1 \oplus a_1\rangle|a_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus a_i\rangle|a_i \oplus a_{i-1}\rangle \right) |z \oplus a_{n-1}\rangle$$

- Thus we have completed the first portion of the decomposed MAJ gate



Step By Step Creation

 - Step 3:
 - apply CCNOT gates to each B_i , A_i and A_{i+1} for $n=0, \dots, n-1$ with A_{i+1} as target





Step By Step Creation

- Step 3:
 - apply CCNOT gates to each B_i , A_i and A_{i+1} for $n=0, \dots, n-1$ with A_{i+1} as target

$$|b_0\rangle|a_0\rangle|b_1 \oplus a_1\rangle|a_1 \oplus c_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus a_i\rangle|a_i \oplus a_{i-1}\rangle \right) |z \oplus a_{n-1}\rangle$$

- Then we apply Toffoli to the rest of the A_i qubits:


$$|b_0\rangle|a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus a_i\rangle|a_i \oplus c_i\rangle \right) |z \oplus s_n\rangle$$

- In short we “transfer” the carry c_i to each A_i qubit



Step By Step Creation

 - Step 4:
 - Apply CNOT gates to each B_i, A_i for $i=n-1, \dots, 1$ with A_{i+1} as control
 - Apply CCNOT gates to B_{i-1}, A_{i-1}, A_i for $i=n-1, \dots, 1$ with A_i as target





Step By Step Creation


- Step 4:
 - apply CNOT gates to each B_i, A_i for $i=n-1, \dots, 1$ with A_{i+1} as control
 - Apply CCNOT gates to B_{i-1}, A_{i-1}, A_i for $i=n-1, \dots, 1$ with A_i as target
- The CNOT acts on the B_i qubit:
 - $b_i \oplus a_i \rightarrow (b_i \oplus a_i) \oplus (a_i \oplus c_i) \rightarrow b_i \oplus c_i$
- Then we reverse the application of the first group of Toffoli gates
- Thus we end up with:

$$|b_0\rangle|a_0\rangle|b_1 \oplus c_1\rangle|a_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus c_i\rangle|a_i \oplus a_{i-1}\rangle \right) |z \oplus s_n\rangle$$



Step By Step Creation

 - Step 5:
 - apply CNOT gates to each $A_i \cdot A_{i+1}$ for $i=1,\dots,n-2$ with A_{i+1} as target





Step By Step Creation

- **Step 5:** apply CNOT gates to each A_i . A_{i+1} for $i=1,\dots,n-2$ with A_{i+1} as **target**
- With this transformation we bring the state of each A_i to the **original value**

$$|b_0\rangle|a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus c_i\rangle|a_i\rangle \right) |z \oplus s_n\rangle$$


- The remaining step will finally proceed with the **sum** of the two components




Step By Step Creation

$$\left(\bigotimes_{i=0}^{n-1} |b_i\rangle |a_i\rangle \right) |z\rangle \rightarrow \left(\bigotimes_{i=0}^{n-1} |s_i\rangle |a_i\rangle \right) |z \oplus s_n\rangle$$

 - Step 6:
 - apply CNOT gates to B_i, A_i for $i = 0, \dots, n-1$ with B_i as target




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have 1




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have $1 + 4$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have $1 + 4 + 25$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have $1 + 4 + 25 + 24$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have $1 + 4 + 25 + 24 + 3$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Depth and Delay

- The **Depth** of the entire circuit is $5N - 3$
- The **Delay** is $13N - 7$ (for $N = 5$ we have 58)
 - In this example we have $1 + 4 + 25 + 24 + 3 + 1 = 58$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have 4




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4 + 25$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4 + 25 + 24$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4 + 25 + 24 + 3$




 


 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost

- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4 + 25 + 24 + 3 + 5 = 65$




 

 (b) quantum implementation of Toffoli gate

Cost Analysis - Size and Quantum Cost


- The **Size** of the circuit is $7N - 6$
- The **Quantum Cost** is $15N - 9$
 - But here we have $4 + 4 + 25 + 24 + 3 + 5 = 65$ (and $15N - 9$ is 66)





Cost Analysis - CNOT

 
- The number of Feynman gates is $5N - 5$
- Here we have 20 CNOT gates





Cost Analysis - CCNOT

 - The number of Toffoli gates is $2N - 1$
- For $N = 5$, we have 9 CCNOT gates





SAPIENZA
UNIVERSITÀ DI ROMA

Thapliyal

2013




Introduction

- The Thapliyal circuit we present is a reversible ripple carry adder
- The design has
 - no input carry
 - no ancilla bits
 - no garbage outputs
- The number of qubits is $2N + 1$
- The carry is computed in the first stage similarly to the Takahashi adder
- A key component is the Peres Gate




Peres Gate

 - The Peres gate has **quantum cost** 4 and **delay** 4Δ






Controlled V and V^+ Gates

 

 
$$V = \frac{1+i}{2} \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & -i \\ 0 & 0 & -i & 1 \end{pmatrix}$$



$$V^+ = \frac{1-i}{2} \begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & i \\ 0 & 0 & i & 1 \end{pmatrix}$$



Thapliyal - Circuit (N = 5)

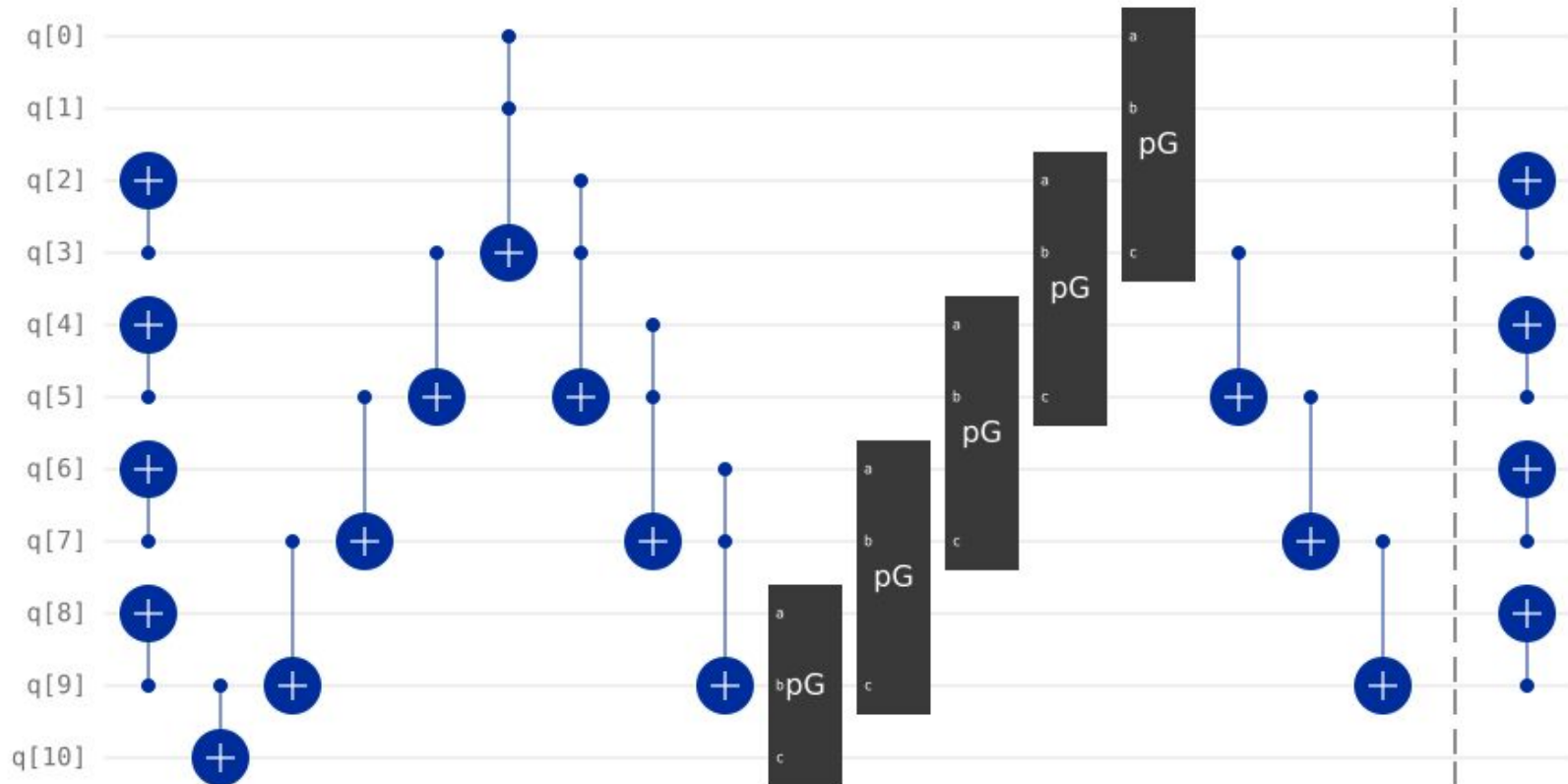




Step By Step Creation

- Step 1:
 - apply CNOT gates to each B_i, A_i for $i=1,..,n-1$ with A_{i+1} as control
- The system state becomes:

$$|b_0\rangle |a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus a_i\rangle |a_i\rangle \right) |z\rangle$$

 


(a) after step 1



Step By Step Creation

- **Step 2:**
 - apply CNOT gates to each A_i, A_{i+1} for $i=n-1, \dots, 1$ with A_i as **control**
- The **system state** becomes:

$$|b_0\rangle |a_0\rangle |b_1 \oplus a_1\rangle |a_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus a_i\rangle |a_i \oplus a_{i-1}\rangle \right) |z \oplus a_{n-1}\rangle$$
- **Step 1** and **2** are the same as the previous adder

 

(b) after step 2


Step By Step Creation

- Step 3:
 - apply CCNOT gates to each A_i, B_i, A_{i+1} for $i=0, \dots, n-2$ with A_{i+1} as target

- The system state becomes:

$$|b_0\rangle |a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus a_i\rangle |a_i \oplus c_i\rangle \right) |z \oplus a_{n-1}\rangle$$

 
- By applying Toffoli gates we obtain the carry bits



(c) after step 3

Step By Step Creation

- **Step 4:**
 - apply Peres gates to each A_i, B_i, A_{i+1} on gate inputs A,B and C for $i=n-1, \dots, 0$
- The **system state** becomes: $|s_0\rangle |a_0\rangle |b_1 \oplus c_1\rangle |a_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus c_i\rangle |a_i \oplus a_{i-1}\rangle \right) |z \oplus s_n\rangle$

 


(a) after step 4



Step By Step Creation

- **Step 4:**
 - apply Peres gates to each A_i, B_i, A_{i+1} on gate inputs A,B and C for $i=n-1, \dots, 0$
- The **system state** becomes: $|s_0\rangle |a_0\rangle |b_1 \oplus c_1\rangle |a_1\rangle \left(\bigotimes_{i=2}^{n-1} |b_i \oplus c_i\rangle |a_i \oplus a_{i-1}\rangle \right) |z \oplus s_n\rangle$
- For example with respect to the **Peres Gate** for A_0, B_0, A_1 we have:
 - $A_0: a_0 \Rightarrow a_0$
 - $B_0: b_0 \Rightarrow b_0 \oplus a_0$
 - $A_1: a_1 \oplus c_1 \Rightarrow a_1 \oplus c_1 \oplus a_0 b_0 \Rightarrow a_1$

 




Step By Step Creation

- Step 5:
 - apply CNOT gates to each A_i, A_{i+1} for $i=1, n-2$ with A_{i+1} as target

- The system state becomes: $|s_0\rangle |a_0\rangle \left(\bigotimes_{i=1}^{n-1} |b_i \oplus c_i\rangle |a_i\rangle \right) |z \oplus s_n\rangle$


- We reverse the transformation on A_{i+1} qubit
- From $|a_i \oplus a_{i-1}\rangle$ to $|a_i\rangle$

 

(b) after step 5

Step By Step Creation

- Step 6:
 - apply CNOT gates to each B_i, A_i for $i=1,\dots,n-1$ with A_i as control
- The circuit is finished and computes the sum $\left(\bigotimes_{i=0}^{n-1} |s_i\rangle |a_i\rangle \right) |z \oplus s_n\rangle$

 


 (c) after step 6



Cost Analysis


- Quantum Cost is $13N - 8$ (with $N = 5$, the value is 57)





Cost Analysis

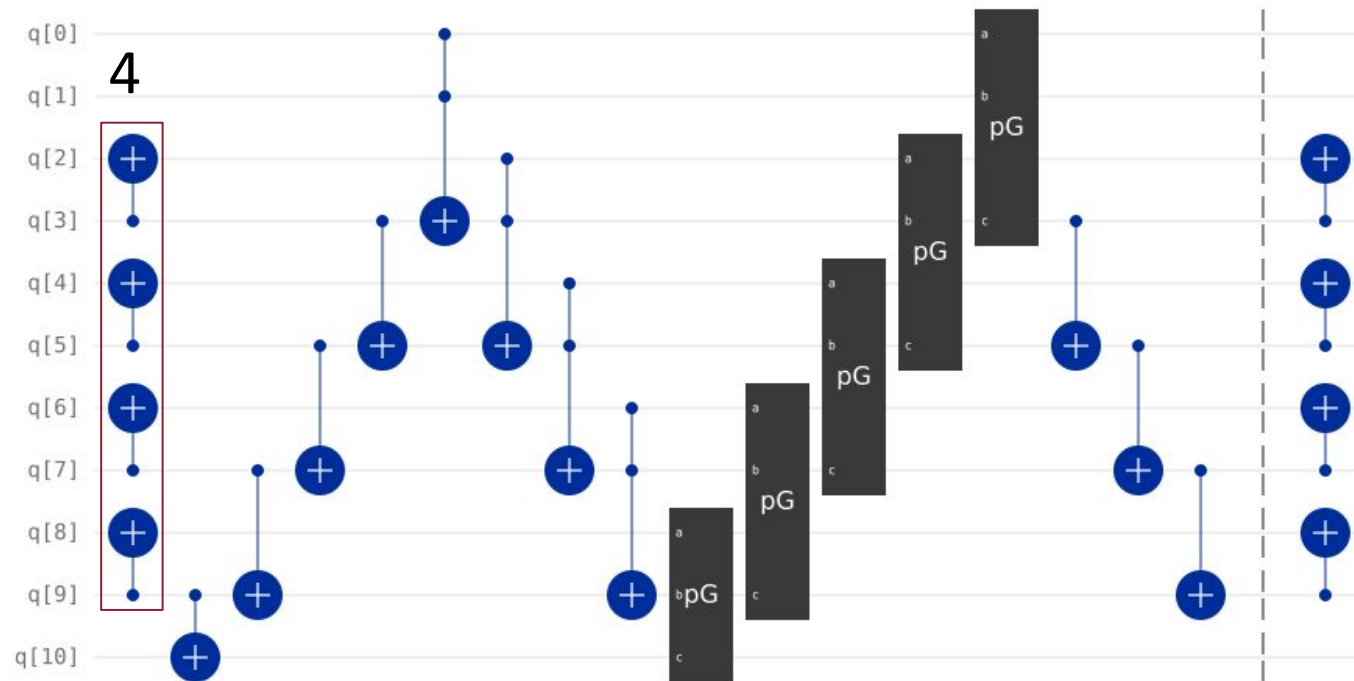
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example: 4





Cost Analysis

 
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example: $4 + 4$





Cost Analysis

 
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example $4 + 4 + 20$





Cost Analysis

 
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example $4 + 4 + 20 + 20$





Cost Analysis

 
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example $4 + 4 + 20 + 20 + 3$





Cost Analysis

 
- **Quantum Cost** is $13N - 8$ (with $N = 5$, the value is 57)
 - But in the example $4 + 4 + 20 + 20 + 3 + 4 = 55$





Cost Analysis

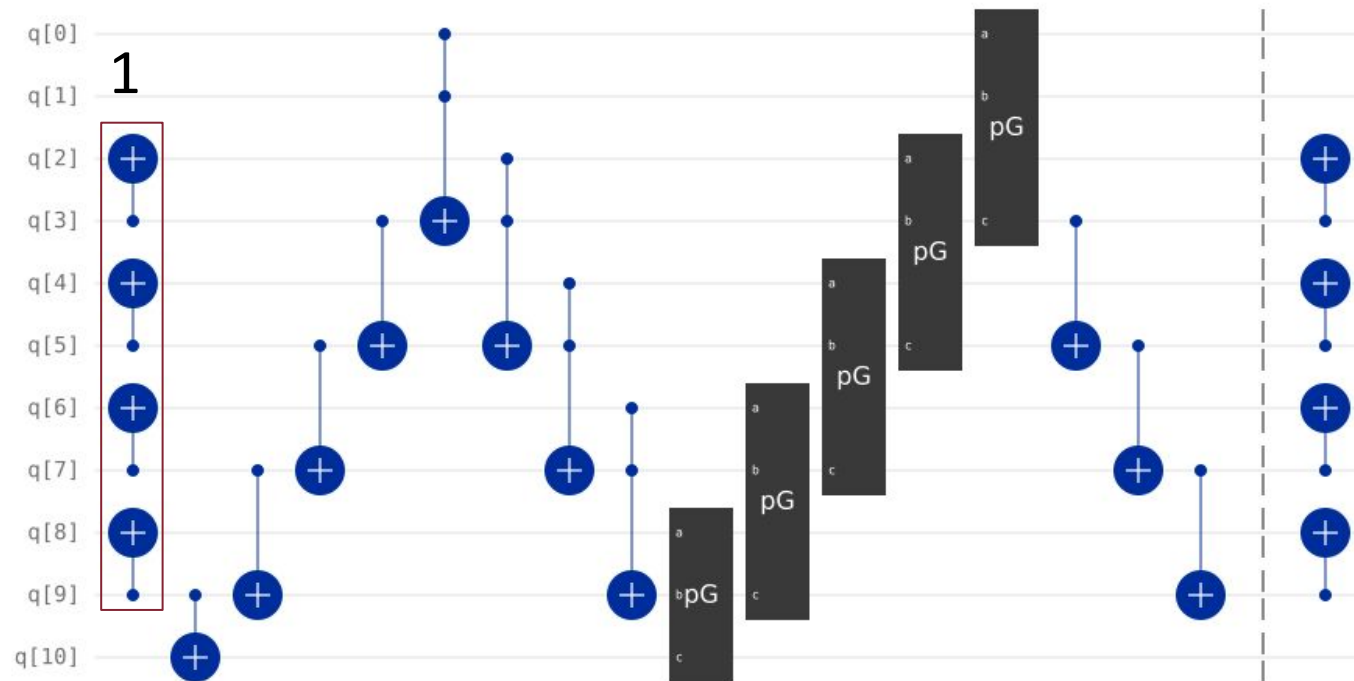
- **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: 1





Cost Analysis

 
- **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: $1 + 4$





Cost Analysis

 
- **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: $1 + 4 + 4 * 5$





Cost Analysis

 
- **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: $1 + 4 + 4 * 5 + 5 * 4$





Cost Analysis

 
- **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: $1 + 4 + 4 * 5 + 5 * 4 + 3$





Cost Analysis

 - **Propagation Delay** is $11N - 4$ (with $N = 5$, we have 51)
 - But in this example: $1 + 4 + 4 * 5 + 5 * 4 + 3 + 1 = 49$





SAPIENZA
UNIVERSITÀ DI ROMA

Comparison



Comparison

- For this brief analysis we chose the following metrics
 - **Quantum Cost**: Number of 1x1 and 2x2 gates in the circuit.
 - 1x1 and 2x2 gates have cost 1 Unit
 - **Delay**: Number of 1x1 and 2x2 gates in the circuit to be executed sequentially.
 - 1x1 and 2x2 gates have 1 delay
 - **Qubit Required**: number of qubits needed
 - **Auxiliary Inputs**: inputs set to constant value
 - **Garbage Outputs**: outputs that cannot be used at the end
 - **Fault Tolerance**: capability of error suppression



Comparison

Adder	Quantum Cost	Delay	Number of Qubits
Nagamani	$12N$	$10N$	$3N + 1$
Gidney	$18N - 2$	$15N - 5$	$3N - 1$
Takahashi	$15N - 9$	$13N - 7$	$2N + 1$
Thapliyal (1)	$13N - 8$	$11N - 4$	$2N + 1$




Comparison

Adder	Ancilla Bits	Garbage Bits	Fault Tolerant	Carry In
Nagamani	4N	0	No	Yes
Gidney	N	0	Yes	No
Takahashi	0	0	No	No
Thapliyal (1)	0	0	No	No




Qubit Requirement Comparison

 




Quantum Cost Comparison

 



Delay Comparison

 



References

- Nagamani, A., Ashwin, S., & Agrawal, V. (2014). [Design of optimized reversible binary adder/subtractor and BCD adder](#). In *2014 International Conference on Contemporary Computing and Informatics (IC3I)* (pp. 774-779).
- Gidney, C. (2018). [Halving the cost of quantum addition](#). *Quantum*, 2, 74.
- Takahashi, Y., Tani, S., & Kunihiro, N. (2010). [Quantum addition circuits and unbounded fan-out](#). *Quantum Info. Comput.*, 10(9), 872–890.
- Thapliyal, H., & Ranganathan, N. (2013). [Design of efficient reversible logic-based binary and BCD adder circuits](#). *J. Emerg. Technol. Comput. Syst.*, 9(3).
- Orts, F., Ortega, G., Combarro, E. F., & Garzón, E. M. (2020). [A review on reversible quantum adders](#). *Journal of Network and Computer Applications*, 170, 102810.
doi:10.1016/j.jnca.2020.102810



SAPIENZA
UNIVERSITÀ DI ROMA

That's all folks!